

Centro de Investigación y de Estudios Avanzados

TAE 2023 – ASIC DESIGN



Convolution Project Report

SoC Design Methodology

Teacher: Rodrigo Jaramillo Ramírez


Student: Juan Antonio Serrano Gómez

Guadalajara, Jalisco, 30/04/2023

PROBLEM DESCRIPTION

We want to implement a convolution coprocessor from scratch, with two using a top-down approach, following the steps seen in our class. This convolution processor will follow the below description, so we can test it in a simulation TB with RAM and ROM memory designs, simulate it's waveform and analyze it's performance.

BLACK BOX

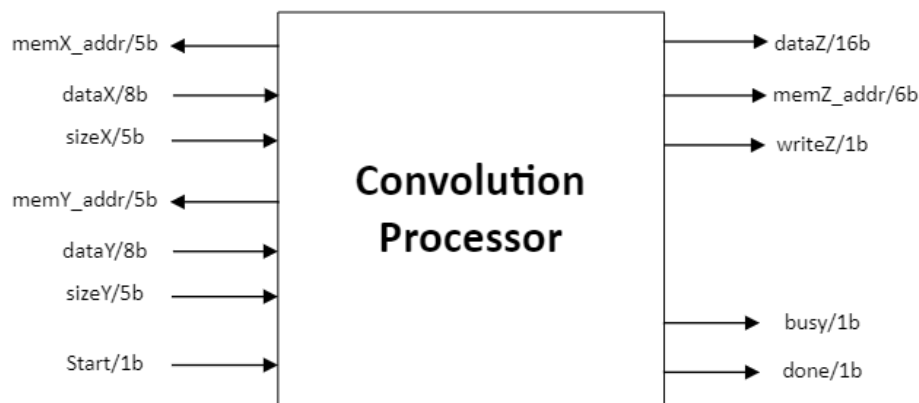

This top level block will require the following I/O ports:

Inputs:

- dataX & dataY = Data stored in memory X and memory Y.
- sizeX & sizeY = Size of the signals stored in each memory.
- memX_addr & memY_addr = Addresses from where to read in memories.
- Start = Start signal.

Outputs:

- Done = One-shot signal to indicate that the operation is complete.
- Busy = Signal indicating the processor is busy.
- WriteZ = Signal to store result in memory Z.
- dataZ = Data to be stored in output memory.
- memZ_addr = Address where output data will be stored.

PSEUDOCODE GENERATION

To develop a pseudocode for our convolution process, we use the formula for convolution reviewed in class, evaluate the specific necessities for its implementation in a HDL design, and create a process that can get, from two input memories, a convolutional output for an output memory:

Convolution Formula:

$$z(n) = \sum_{-\infty}^{\infty} x[k]y[n-k]$$

Given that we want to do a sweep for n and k, we have to avoid the conditions where the addresses fall outside the sizes of our memory vectors. I found the optimal evaluation conditions to be: $(n < Zsize)$ and $(n \geq k)$. Finally, we have to consider the I/O requirements. This results in the following pseudocode:

Pseudocode
1.- While Start = 0; 2.- End While; 3.- Busy = 1; 4.- Zsize = SizeX+SizeY-1; 5.- for n = 0 to (n < Zsize) 6.- for k = 0 to (n >= k) 7.- memX_addr = k; 8.- memY_addr = n-k; 9.- reg_Z = reg_Z+dataX+dataY; 10.- End For 11.- memZ_addr = n; 12.- dataZ = reg_Z; 13.- WriteZ=1 14.- WriteZ=0 15.- reg_Z = 0; 16.- End For 17.- busy = 0; 18.- done = 1; 19.- done = 0; 19.- If Start = 1 21.- goto 1 22.- Else goto 19

PSEUDOCODE VALIDATION

In order to validate the functionality of our pseudocode, we implent it in a C program, using 3 arrays as the memories (two input memories and one ouput memory). We also ad dan algorithm to calculate the input memory (array) sizes, so as to improve the Flow of the validation:

Validación del pseudocódigo en C

```
// Variable Declaration
int data_X, data_Y;
int size_X, size_Y;
int memY__addr, memX_addr, memZ_addr;
int data_Z;
int Z_size, n, k, i,;
int reg_Z = 0;


//Memory declaration
int memY[3] = {2, -1, 0};
int memX[10] = {-1, 0, 1, 4, 6, 7, -8, 4, 5, -2};
int memZ[64];

int main(void) {
//Wait for start input
while(!start){
    printf("Waiting for Start 1:" );
    scanf("%c", &start);
}
//Vectors X, Y & Z Size Calculation
int size_X = sizeof(memX) / sizeof(memX[0]);
int size_Y = sizeof(memY) / sizeof(memY[0]);

Z_size = size_X + size_Y - 1;


printf("Size Z: %d \n", size_X);
// Convolutional Process
for(n=0; n < Z_size; n++) {
    for(k=0; k <= n; k++){
        if((k < size_X) && ((size_Y-1) >= (n-k)))
            reg_Z = reg_Z + memX[k]*memY[n-k];
    }
    memZ[n] = reg_Z;
    reg_Z = 0;
}
// Print Z Memory Locations
for(i=0; i < Z_size; i++){
    printf("z[%i]: %i \n", i, memZ[i]);
    sleep(1);
}
}
```

ASM DIAGRAM

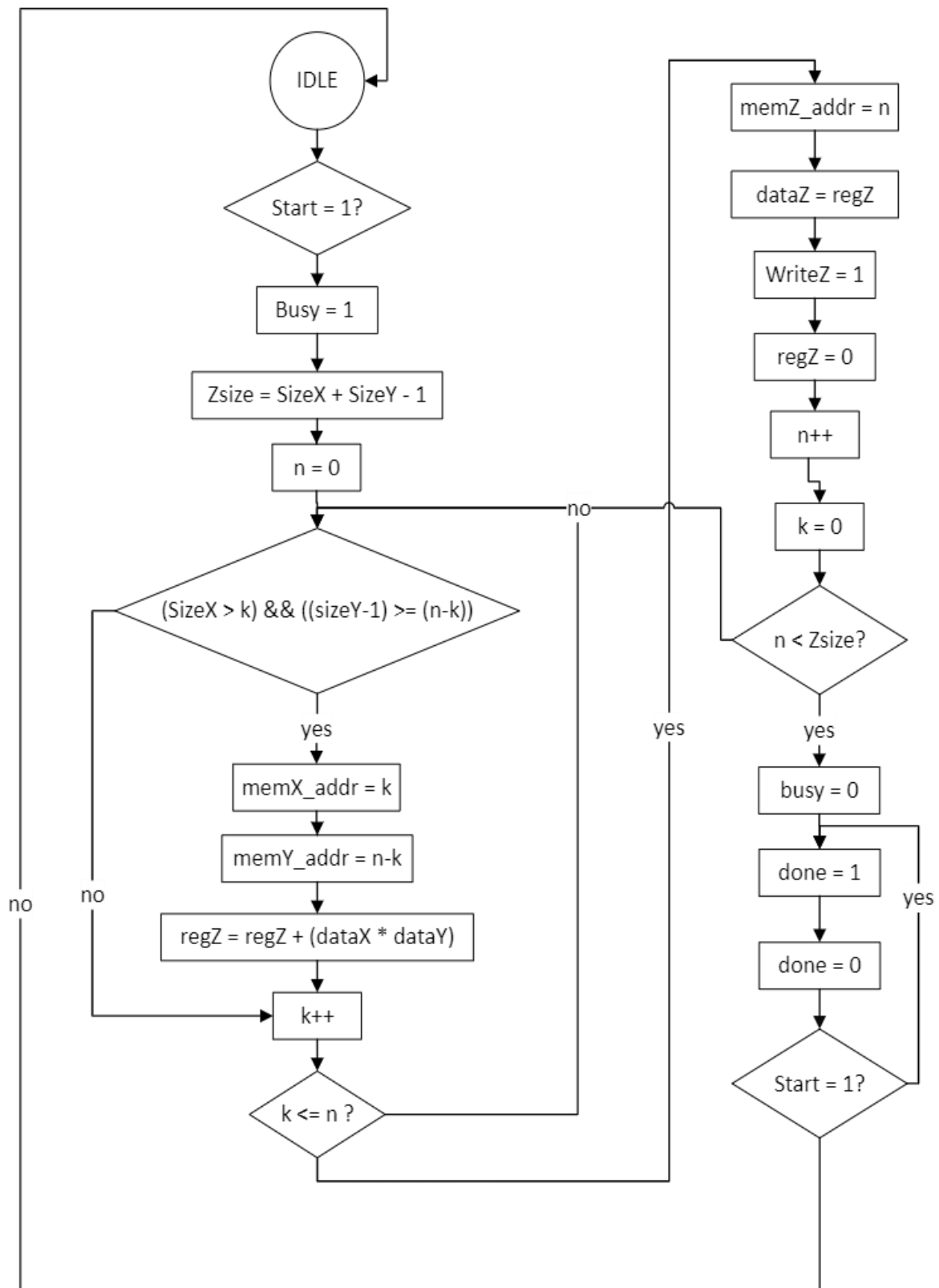


From this ASM diagram, we can start generating the “optimum” Building Blocks for the datapath:


BUILDING BLOCKS GENERATION

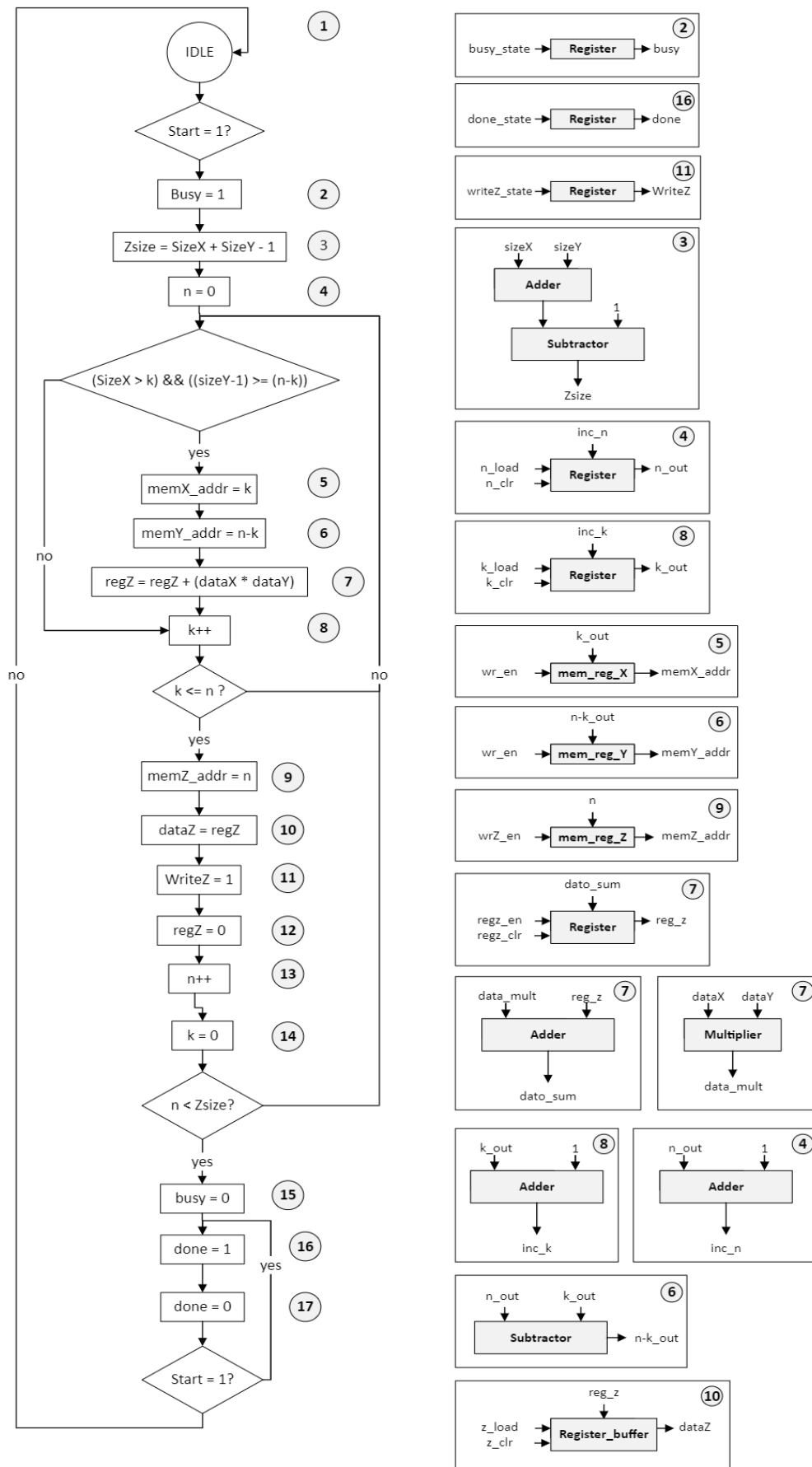


BUILDING BLOCKS OPTIMIZATION

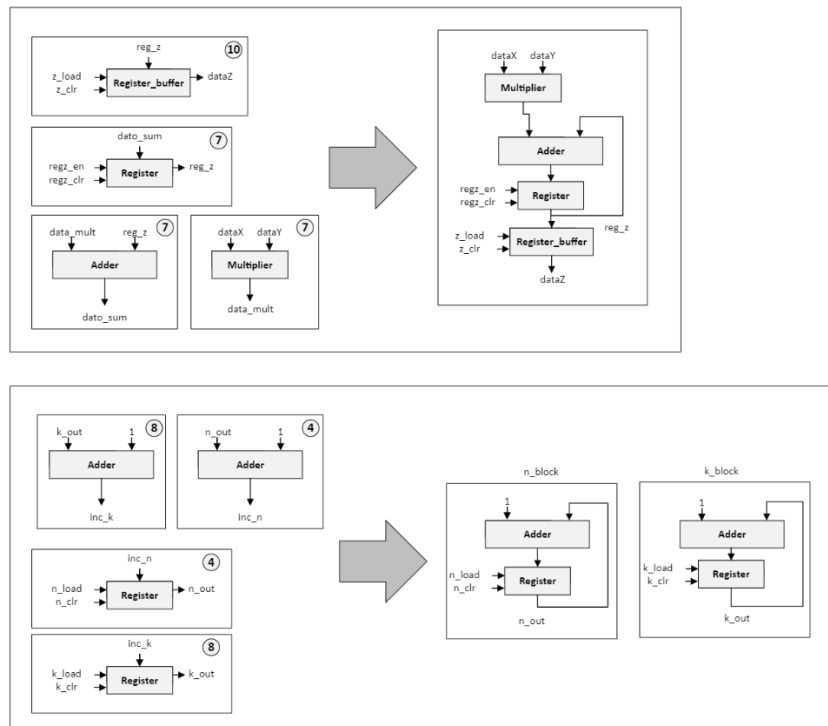

DATAPATH CONSTRUCTION

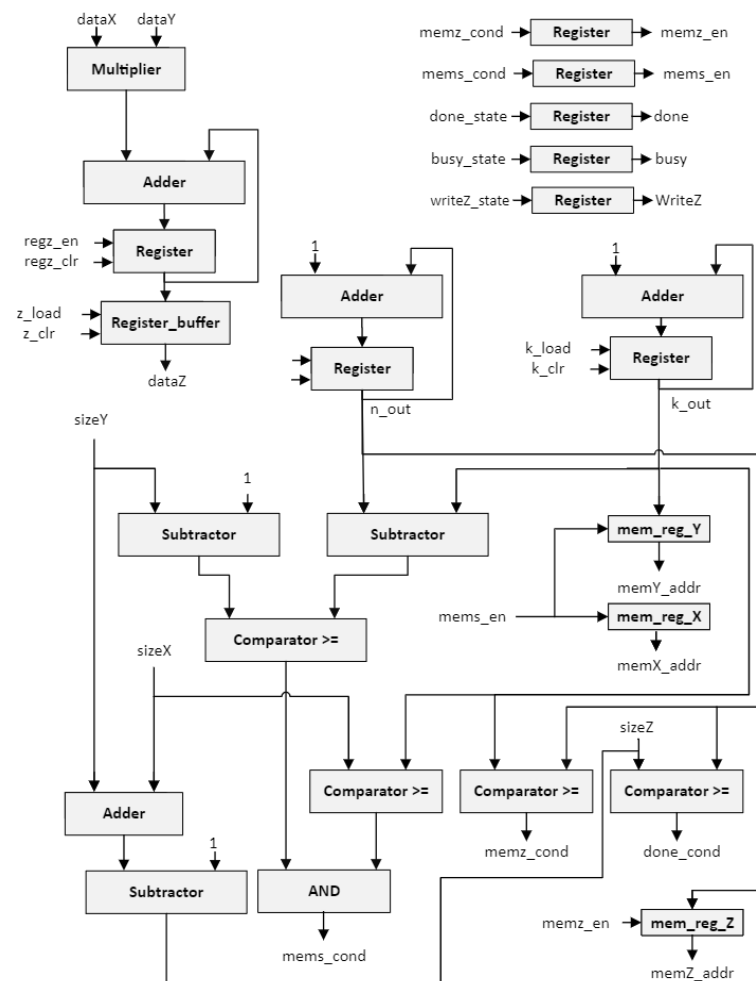


CONTROL SIGNALS FOR DATAPATH

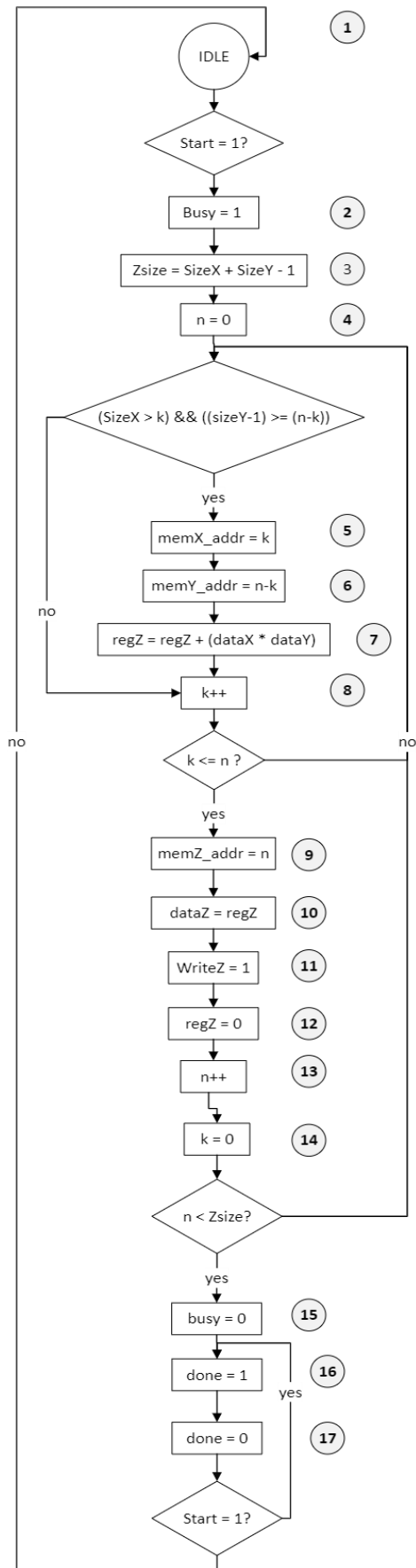


Control FSM		
State	Input/Value	Output/Value
1	Start/0	
2	Start/1	busy_state/1
3		ini_State/1
4		n_clear/1
5	done_i/0 mems_cond/1 memz_cond/1	
6		mems_en/1
7		d_get/1 regz_load/1
8		k_load/1
9	memZ_cond	
10		memz_en/1
11		wr_z/1 z_load/1
12		regz_clr/1
13		n_load/1
14		k_clr/1
15		busy_state/0
16		done_state/1
17	Start/0	done_state/0

FSM: (inputs and outputs)

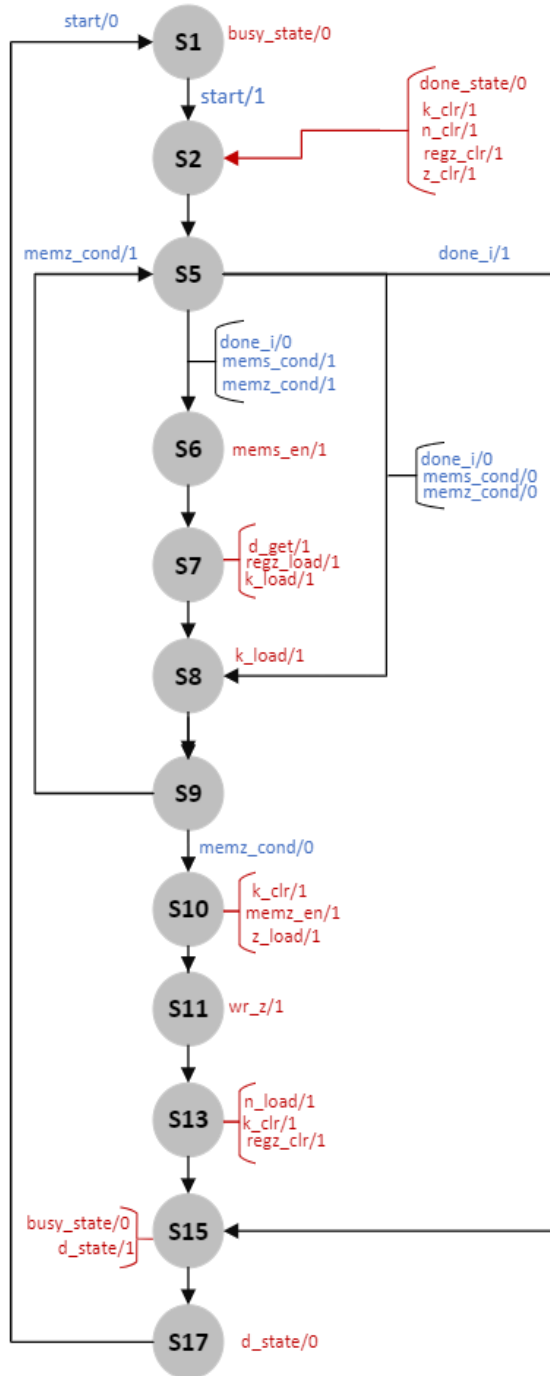


Control FSM		
State	Input/Value	Output/Value
1	Start/0	
2	Start/1	busy_state/1
3		ini_State/1
4		n_clear/1
5	done_i/0 mems_cond/1 memz_cond/1	
6		mems_en/1
7		d_get/1 regz_load/1
8		k_load/1
9	memZ_cond	
10		memz_en/1
11		wr_z/1 z_load/1
12		regz_clr/1
13		n_load/1
14		k_clr/1
15		busy_state/0
16		done_state/1
17	Start/0	done_state/0

DESIGN CORRECTIONS AND IMPROVEMENTS:

 

FPGA SIMULATION AND SYNTHESIS

TOP LEVEL SCHEMATIC:

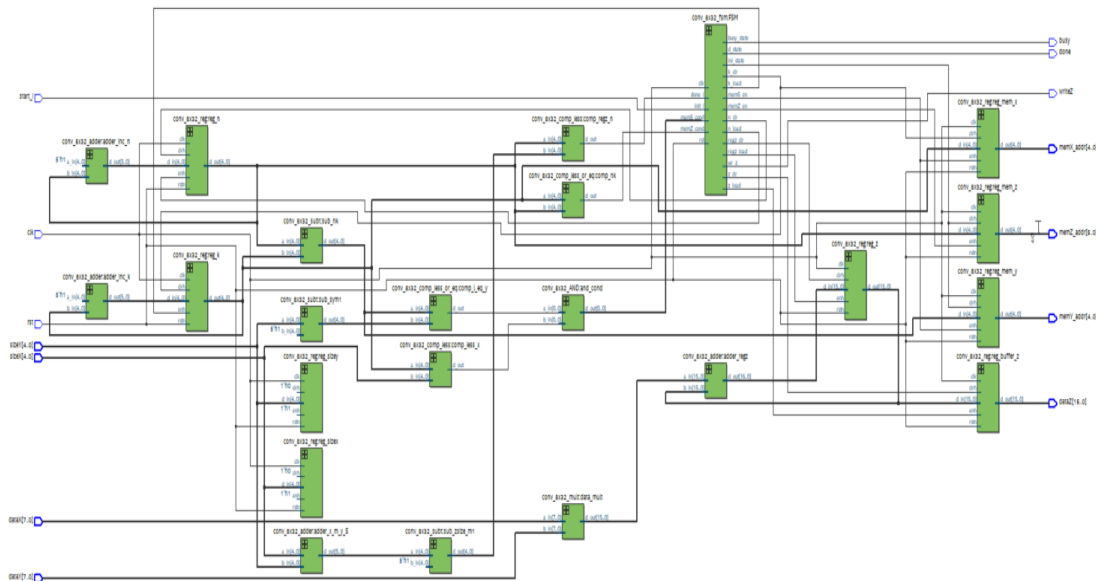

MEMORY FILE GENERATOR:

Memory File Generator (Matlab .m code)

```
%Write X size
Xsize = 5;

%Write Y size
Ysize = 10;

x = randi([0 17],1,Xsize);
y = randi([0 17],1,Ysize);







%Write file location
fileID = fopen('C:/juanquant/conv_proy/mem_X.txt','w');
fprintf(fileID,'%02X\r',x);
fclose(fileID);


%Write file location
fileID = fopen('C:/juanquant/conv_proy/mem_Y.txt','w');
fprintf(fileID,'%02X\r',y);
fclose(fileID);
```

The screenshot shows the Logic Analyzer tool with the following signals and data:

Signal	Value
/conv_8x32_tb/clk	0
/conv_8x32_tb/rstn	0
/conv_8x32_tb/init_i	0
/conv_8x32_tb/busy	0
/conv_8x32_tb/writeZ	0
/conv_8x32_tb/done	0
/conv_8x32_tb/data_X	xxxxxxxx
/conv_8x32_tb/data_Y	xxxxxxxx
/conv_8x32_tb/data_Z	0000000000000000
/conv_8x32_tb/memX_addr	000000
/conv_8x32_tb/memY_addr	000000
/conv_8x32_tb/memZ_addr	000000

The timing diagram shows the signals over time. The clock signal (clk) is a periodic square wave. The reset signal (rstn) is a single pulse. The initialization signal (init_i) is a single pulse. The busy signal (busy) is a single pulse. The write enable signal (writeZ) is a single pulse. The done signal (done) is a single pulse. The data outputs (data_X, data_Y, data_Z) are shown as hexadecimal values. The time scale is 500 ns, and the cursor is at 0.00 ns.

      

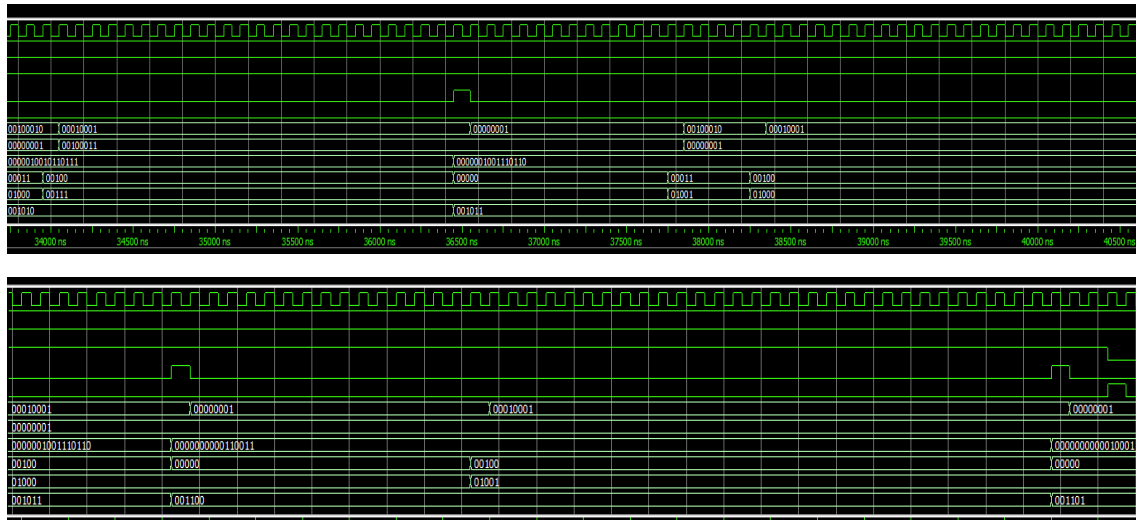

AREA

Family	Cyclone V
Device	5CSEMA5F31C6
Timing Models	Final
Logic utilization (in ALMs)	50 / 32,070 (< 1 %)
Total registers	85
Total pins	64 / 457 (14 %)
Total virtual pins	0
Total block memory bits	0 / 4,065,280 (0 %)
Total DSP Blocks	1 / 87 (1 %)
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total PLLs	0 / 6 (0 %)
Total DLLs	0 / 4 (0 %)

MAXIMUM FREQUENCY


Slow 1100 mV 85C model

Slow 1100mV 85C Model Fmax Summary				
<<Filter>>				
	Fmax	Restricted Fmax	Clock Name	Note
1	326.37 MHz	326.37 MHz	clk	

Slow 1100 mV 0C Model

Slow 1100mV 0C Model Fmax Summary				
<<Filter>>				
	Fmax	Restricted Fmax	Clock Name	Note
1	313.38 MHz	313.38 MHz	clk	

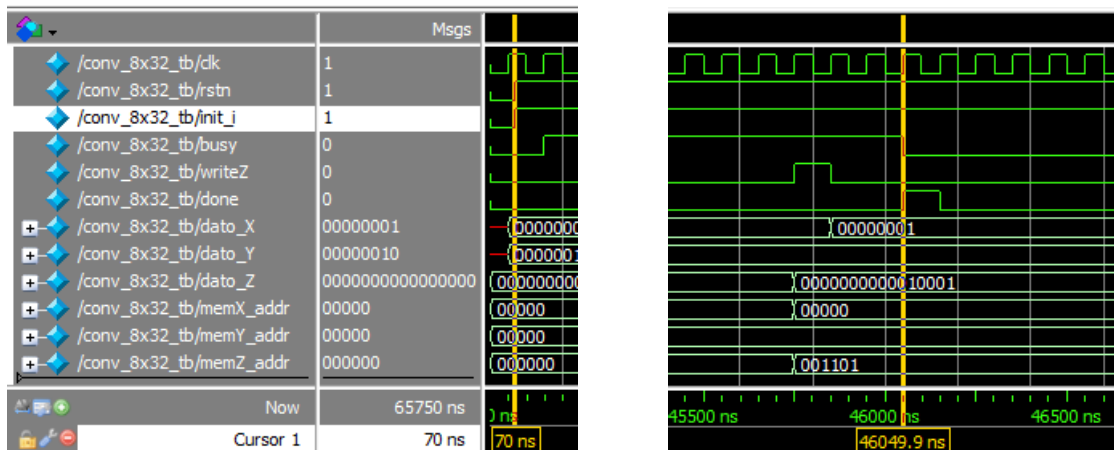NUMBER OF CLOCK CYCLES FOR: Xsize = 5 and Ysize = 10



R.- 459 - 460 Clock Cycles, depending on whether you start counting from the first edge before the start condition, or after (meaning, if we start from the IDLE state or the INICIO state).